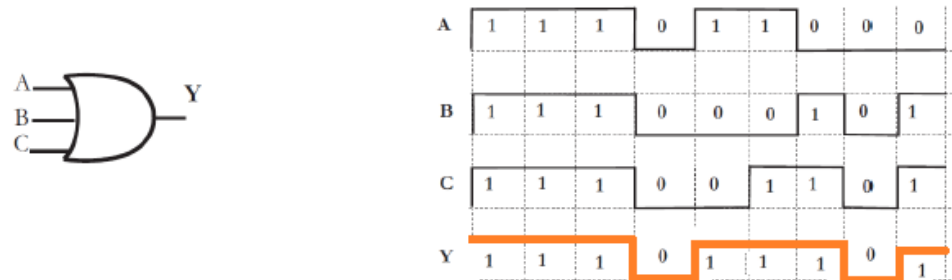



[2.1] Given the pulse train sent to the input A of an OR gate, draw its output pulse train.




[2.2] Given the pulse train sent to the input A, B and C of an OR gate, draw its output pulse train.



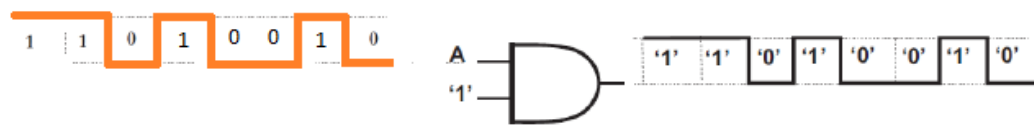
[2.3] The output of an AND gate shows the following pulse train. Draw the corresponding signal at input A.



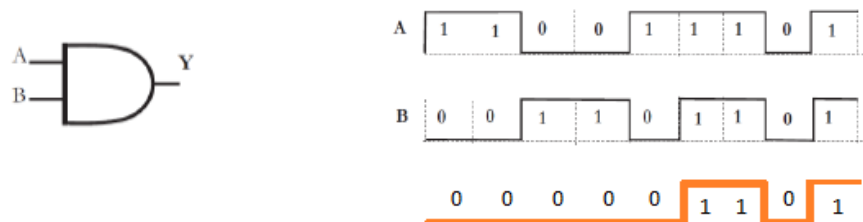
[2.4] Given the following pulse trains sent to the 2 inputs A and B of an AND gate, find the output pulse train.



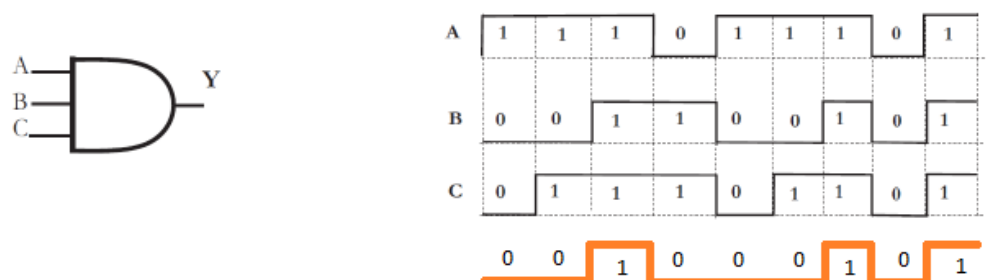
[2.5] Given the following pulse trains sent to the 3 inputs A, B and C of an AND gate, find the output pulse train.




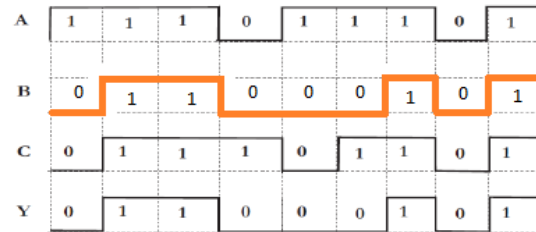
- [2.6] The output Y and the inputs A and C of an AND gate have the following pulse trains. Draw the corresponding signal at input B .



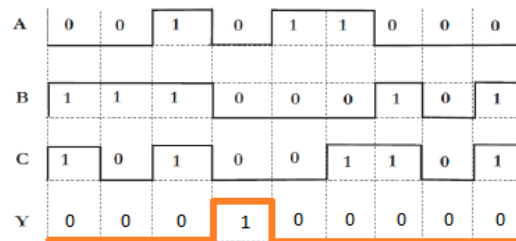- [2.7] Given the following pulse trains sent to the 3 inputs A , B and C of a NOR gate, find the output pulse train.



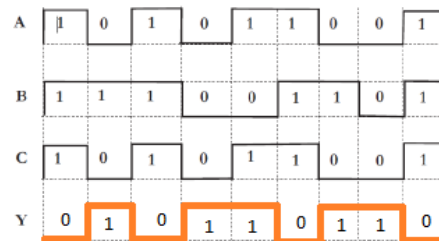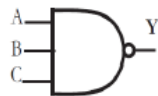- [2.8] Given the following pulse trains sent to the 3 inputs A , B and C of a NAND gate, find the output pulse train.



- [2.9] Demonstrate the validity of the following identities by means of truth tables :

(a) DeMorgan's theorem for three variables: $(x + y + z)' = x'y'z'$ and $(xyz)' = x' + y' + z'$

x	y	z	$x + y + z$	$(x + y + z)'$	x'	y'	z'	$x'y'z'$
0	0	0	0	1	1	1	1	1
0	0	1	1	0	1	1	0	0
0	1	0	1	0	1	0	1	0
0	1	1	1	0	1	0	0	0
1	0	0	1	0	0	1	1	0
1	0	1	1	0	0	1	0	0
1	1	0	1	0	0	0	1	0
1	1	1	1	0	0	0	0	0
x	y	z	(xyz)	$(xyz)'$	x'	y'	z'	$x' + y' + z'$
0	0	0	0	1	1	1	1	1
0	0	1	0	1	1	1	0	1
0	1	0	0	1	1	0	1	1
0	1	1	0	1	1	0	0	1
1	0	0	0	1	0	1	1	1
1	0	1	0	1	0	1	0	1
1	1	0	0	1	0	0	1	1
1	1	1	1	0	0	0	0	0

(b) The distributive law: $x + yz = (x + y)(x + z)$

x y z	$x+yz$	$(x+y)$	$(x+z)$	$(x+y)(x+z)$
0 0 0	0	0	0	0
0 0 1	0	0	1	0
0 1 0	0	1	0	0
0 1 1	1	1	1	1
1 0 0	1	1	1	1
1 0 1	1	1	1	1
1 1 0	1	1	1	1
1 1 1	1	1	1	1

(c) The distributive law: $x(y+z) = xy + xz$

x y z	$x(y+z)$	xy	xz	$xy + xz$
0 0 0	0	0	0	0
0 0 1	0	0	0	0
0 1 0	0	0	0	0
0 1 1	0	0	0	0
1 0 0	0	0	0	0
1 0 1	1	0	1	1
1 1 0	1	1	0	1
1 1 1	1	1	1	1

(d) The associative law: $x + (y + z) = (x + y) + z$

x y z	$y+z$	$x+(y+z)$	$(x+y)$	$(x+y)+z$
0 0 0	0	0	0	0
0 0 1	1	1	0	1
0 1 0	1	1	1	1
0 1 1	1	1	1	1
1 0 0	0	1	1	1
1 0 1	1	1	1	1
1 1 0	1	1	1	1
1 1 1	1	1	1	1

(e) The associative law and $x(yz) = (xy)z$

x y z	yz	$x(yz)$	xy	$(xy)z$
0 0 0	0	0	0	0
0 0 1	0	0	0	0
0 1 0	0	0	0	0
0 1 1	1	0	0	0
1 0 0	0	0	0	0
1 0 1	0	0	0	0
1 1 0	0	0	1	0
1 1 1	1	1	1	1

[2.10] Simplify the following Boolean expressions to a minimum number of literals :

(a) $xy + xy'$

$$=xy + xy' = x(y + y') = x$$

(b) $(x + y)(x + y')$

$$=(x + y)(x + y') = x + yy' = x(x + y') + y(x + y') = xx + xy' + xy + yy' = x$$

(c) $xyz + x'y + xyz'$

$$=xyz + x'y + xyz' = xy(z + z') + x'y = xy + x'y = y$$

(d) $(A + B)'(A' + B)'$

$$=(A + B)'(A' + B') = (A'B')(A B) = (A'B')(BA) = A'(B'BA) = 0$$

(e) $(a + b + c')(a'b' + c)$

$$\begin{aligned} &= a a' b' + a c + b a' b' + b c + c' a' b' + c' c \\ &= (a a') b' + a c + (b b') a' + b c + c' a' b' + 0 \\ &= b'(0) + a c + a'(0) + b c + c' a' b' \\ &= a c + b c + c' a' b' \end{aligned}$$

[2.11] Simplify the following Boolean expressions to a minimum number of literals :

(a) $ABC + A'B + ABC'$

$$ABC + A'B + ABC' = AB + A'B = B$$

(b) $x'yz + xz$

$$x'yz + xz = (x'y + x)z = z(x + x')(x + y) = z(x + y)$$

(c) $(x + y)'(x' + y')$

$$(x + y)'(x' + y') = x'y'(x' + y') = x'y'$$

(d) $xy + x(wz + wz')$

$$xy + x(wz + wz') = x(y + wz + wz') = x(w + y)$$

[2.12] Reduce the following Boolean expressions to the indicated number of literals :

(a) $A'C' + ABC + AC'$ to three literals

$$A'C' + ABC + AC' = C' + ABC = (C + C')(C' + AB) = AB + C'$$

(b) $(x'y' + z)' + z + xy + wz$ to three literals

$$\begin{aligned} (x'y' + z)' + z + xy + wz &= (x'y')'z' + z + xy + wz = [(x + y)z' + z] + xy + wz = \\ &= (z + z')(z + x + y) + xy + wz = z + wz + x + xy + y = z(1 + w) + x(1 + y) + y = x + y + z \end{aligned}$$

(c) $A'B(D' + C'D) + B(A + A'CD)$ to one literal


$$\begin{aligned} A'B(D' + C'D) + B(A + A'CD) &= B(A'D' + A'C'D + A + A'CD) \\ &= B(A'D' + A + A'D(C + C')) = B(A + A'(D' + D)) = B(A + A') = B \end{aligned}$$

(d) $(A' + C)(A' + C')(A + B + C'D)$ to four literals


$$\begin{aligned} (A' + C)(A' + C')(A + B + C'D) &= (A' + CC')(A + B + C'D) = A'(A + B + C'D) \\ &= AA' + A'B + A'C'D = A'(B + C'D) \end{aligned}$$

[2.13] Draw logic diagrams of the circuits that implement the original and simplified expressions in Problem 2.11.


a)

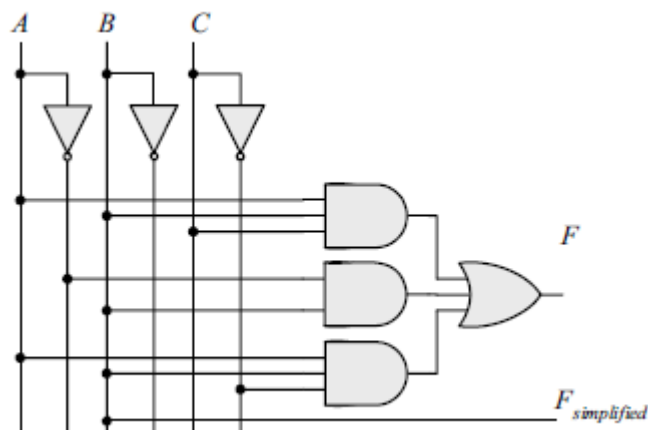


b)

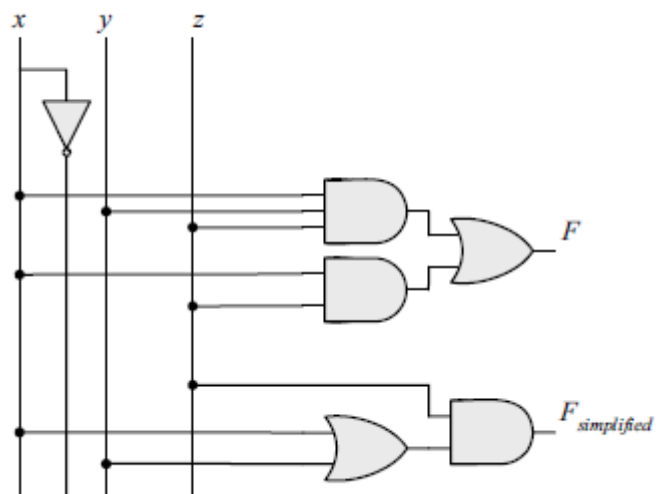

c)

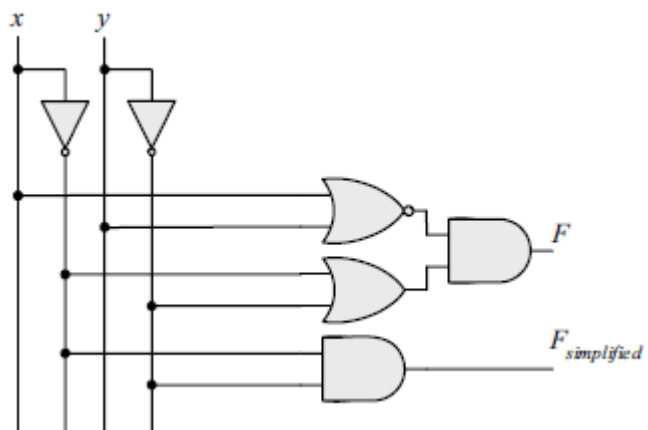

d)

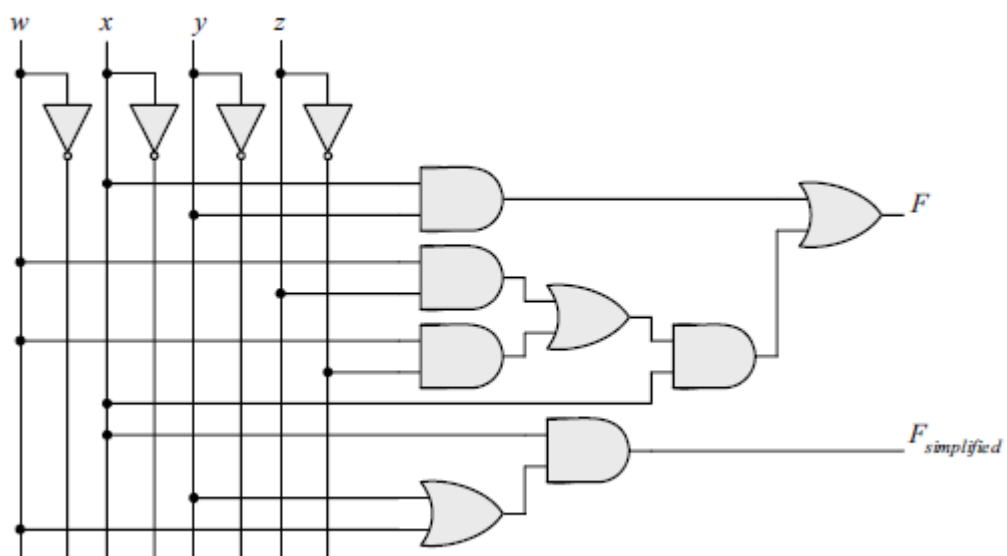

[2.14] Find the complement of the following expressions :

(a) $xy' + x'y$

$$F' = (xy' + x'y)' = (xy')'(x'y)' = (x' + y)(x + y') = xy + x'y'$$

(b) $(a + c)(a + b')(a' + b + c')$

$$F' = (a'c') + (a'b) + (ab'c)$$

(c) $z + z'(v'w + xy)$

$$F' = z'z + (v + w')(x' + y')$$

[2.15] We can perform logical operations on strings of bits by considering each pair of corresponding bits separately (called bitwise operation). Given two eight - bit strings A = 10110001 and B = 10101100, evaluate the eight - bit result after the following logical operations :

(a) AND (b) OR (c) XOR

$$A = 1011_0001$$

$$B = 1010_1100$$


$$(a) A \text{ AND } B = 1010_0000$$

$$(b) A \text{ OR } B = 1011_1101$$


$$(c) A \text{ XOR } B = 0001_1101$$

[2.16] Draw logic diagrams to implement the following Boolean expressions :


(a) $y = [(u + x')(y' + z)]$

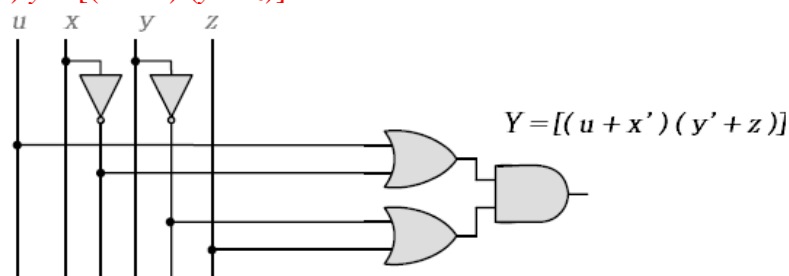


(b) $y = (u \otimes y)' + x$

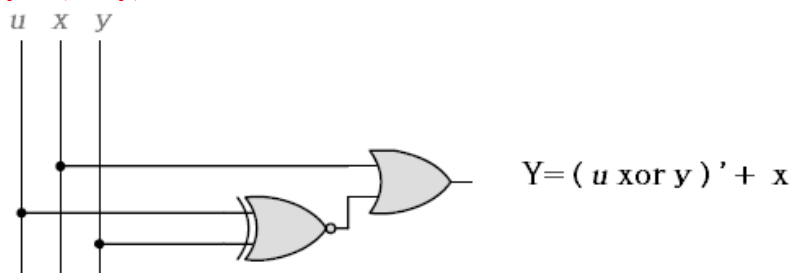

(c) $y = (u' + x')(y + z')$

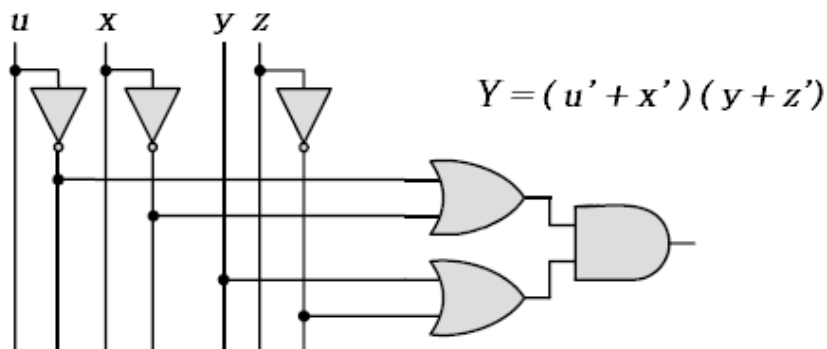


(f) $y = u + x + x'(u + y')$

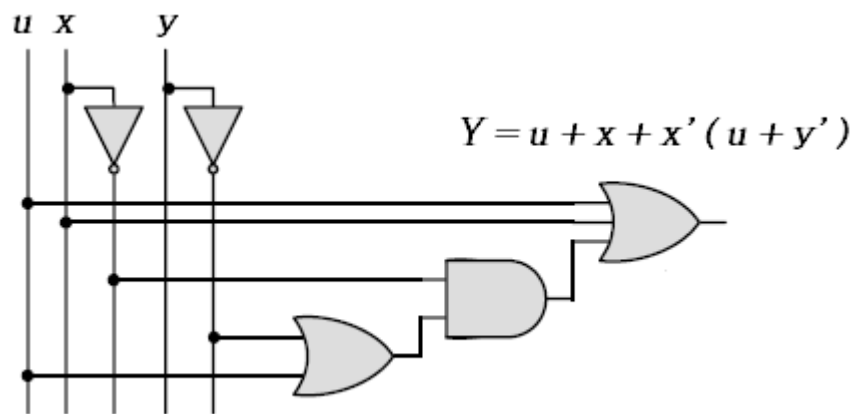


[2.17] Implement the Boolean function

$$F = xy + x'y' + y'z$$


(a) With AND, OR, and inverter gates

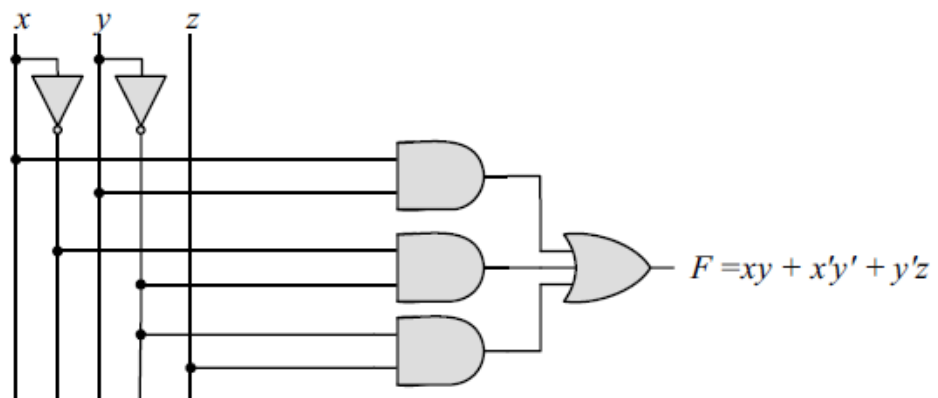


(b) With OR and inverter gates

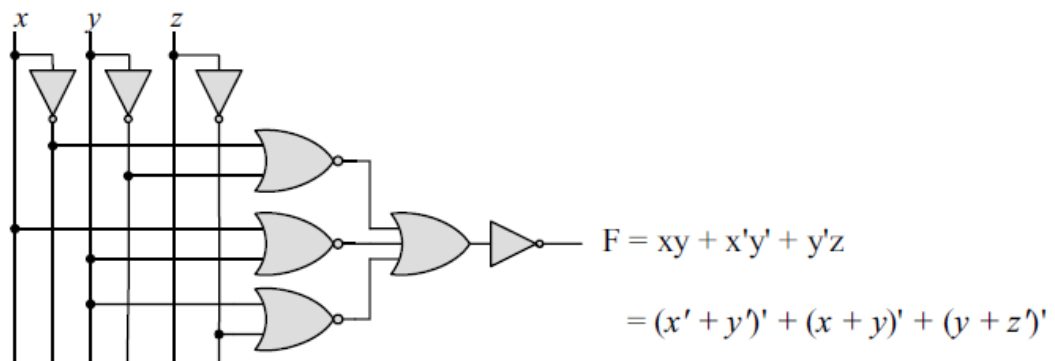


(c) With AND and inverter gates

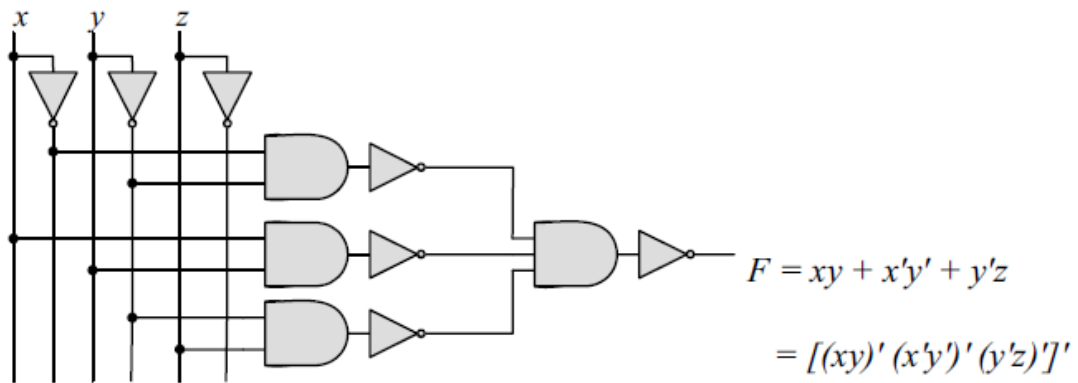

(d) With NAND and inverter gates

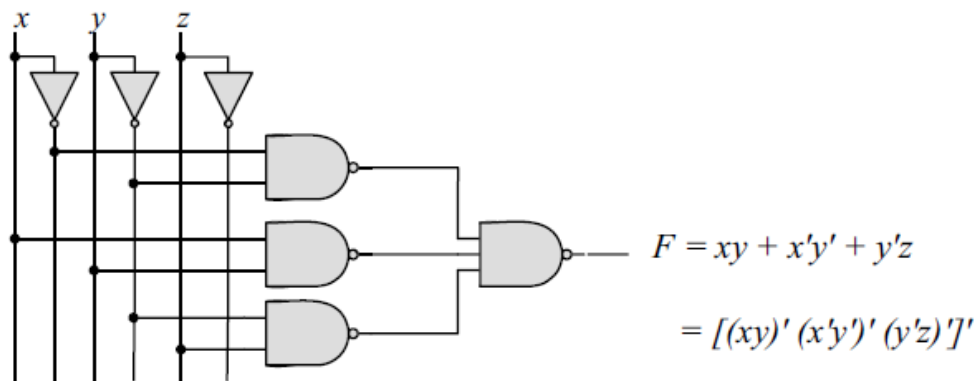

(e) With NOR and inverter gates

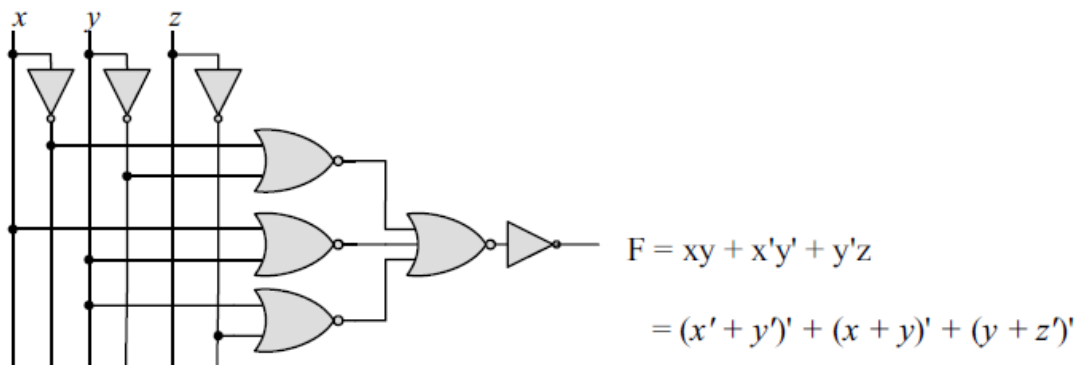

[2.18] Simplify the following Boolean functions T_1 and T_2 to a minimum number of literals :

A	B	C	T_1	T_2
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

$$(a) T1 = A'B'C' + A'B'C + A'BC' = A'B'(C' + C) + A'C'(B' + B) = A'B' + A'C' = A'(B' + C')$$

$$(b) T2 = T1' = A'BC + AB'C' + AB'C + ABC' + ABC \\ = BC(A' + A) + AB'(C' + C) + AB(C' + C) \\ = BC + AB' + AB = BC + A(B' + B) = A + BC$$

$$\Sigma(3, 5, 6, 7) = \prod(0, 1, 2, 4)$$

$$T1 = A'B'C' + A'B'C + A'BC'$$

$$T1 = A'B' A'C' = A'(B' + C')$$

$$T2 = A'BC + AB'C' + AB'C + ABC' + ABC$$

[2.19] Obtain the truth table of the following functions, and express each function in sum-of-minterms and product-of-maxterms form :

$$(a) (b + cd)(c + bd)$$

$$(a) (b + cd)(c + bd) = cd + cb + cbd + bd = \Sigma(3, 5, 6, 7) = \prod(0, 1, 2, 4)$$

$$(b) (cd + b'c + bd')(b + d)$$

$$(cd + b'c + bd')(b + d) = bcd + bb'c + bbd' + cdd + b'cd + bd'd \\ = bcd + 0 + bd' + cd + b'cd + 0 \\ = \Sigma(3, 4, 6, 7) = \prod(0, 1, 2, 5)$$

[2.20] For the Boolean function

$$F = xy'z + x'y'z + w'xy + wx'y + wxy$$


(a) Obtain the truth table of F .

$$F = xy'z + x'y'z + w'xy + wx'y + wxy$$

w x y z	F
0 0 0 0	0
0 0 0 1	1
0 0 1 0	0
0 0 1 1	0
0 1 0 0	0
0 1 0 1	1
0 1 1 0	1
0 1 1 1	1
1 0 0 0	0
1 0 0 1	1
1 0 1 0	1
1 0 1 1	1
1 1 0 0	0
1 1 0 1	1
1 1 1 0	1
1 1 1 1	1

$$F = \Sigma(1, 5, 6, 7, 9, 10, 11, 13, 14, 15)$$

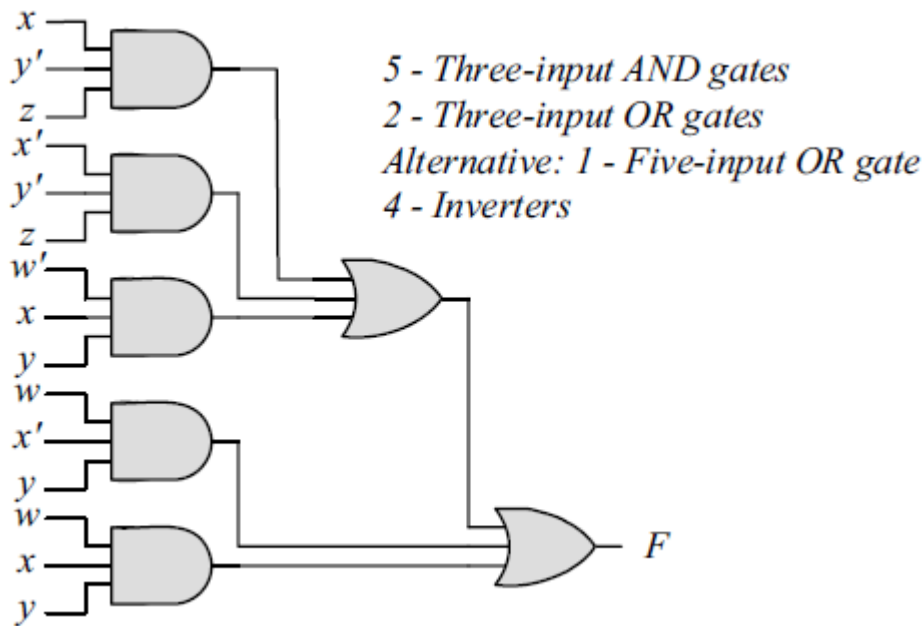(b) Draw the logic diagram, using the original Boolean expression.



(c) Use Boolean algebra to simplify the function to a minimum number of literals.

$$F = xy'z + x'y'z + w'xy + wx'y + wxy = y'z + xy + wy = y'z + y(w + x)$$

[2.21] Express the following function as a sum of minterms and as a product of maxterms :

$$F(A, B, C, D) = B'D + A'D + BD$$

$$F = B'D + A'D + BD$$

ABCD	ABCD	ABCD
-B'-D	A'--D	-B-D
0001 = 1	0001 = 1	0101 = 5
0011 = 3	0011 = 3	0111 = 7
1001 = 9	0101 = 5	1101 = 13
1011 = 11	0111 = 7	1111 = 15

$$F = \sum(1, 3, 5, 7, 9, 11, 13, 15) = \prod(0, 2, 4, 6, 8, 10, 12, 14)$$

[2.22] Express the complement of the following functions in sum-of-minterms form :

(a) $F(A, B, C, D) = \sum(2, 4, 7, 10, 12, 14)$

$$F(A, B, C, D) = \sum(2, 4, 7, 10, 12, 14) = \prod(0, 1, 3, 5, 6, 8, 9, 11, 13, 15)$$

(b) $F(x, y, z) = \prod(3, 5, 7)$

$$F(x, y, z) = \prod(3, 5, 7) = \sum(3, 5, 7)$$

[2.23] Convert each of the following to the other canonical form :

(a) $F(x, y, z) = \sum(1, 3, 5)$

$$F(x, y, z) = \sum(1, 3, 5) = \prod(0, 2, 4, 6, 7)$$

(b) $F(A, B, C, D) = \prod(3, 5, 8, 11)$

$$F(A, B, C, D) = \prod(3, 5, 8, 11) = \sum(0, 1, 2, 4, 6, 7, 9, 10, 12, 13, 14, 15)$$

[2.24] Convert each of the following expressions into sum of products and product of sums :

(a) $(u + xw)(x + u'v)$

$$= ux + uu'v + xxw + xwu'v$$

$$= ux + xw + xwu'v$$

(b) $x' + x(x + y')(y + z')$


$$= (x' + x)[x' + (x + y')(y + z')]$$

$$= (x' + x + y')(x' + y + z')$$


$$= x' + y + z'$$

[2.25] Draw the logic diagram corresponding to the following Boolean expressions without simplifying them :


(a) $BC' + AB + ACD$

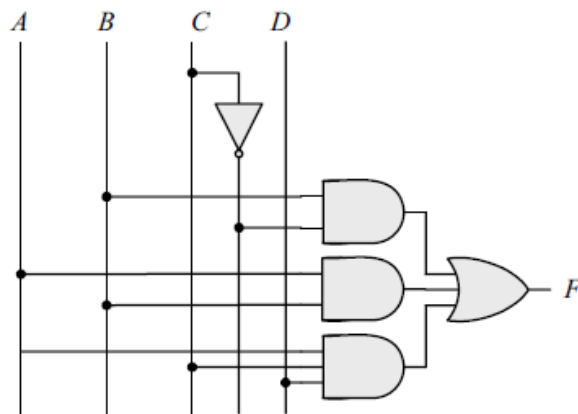


(b) $(A + B)(C + D)(A' + B + D)$

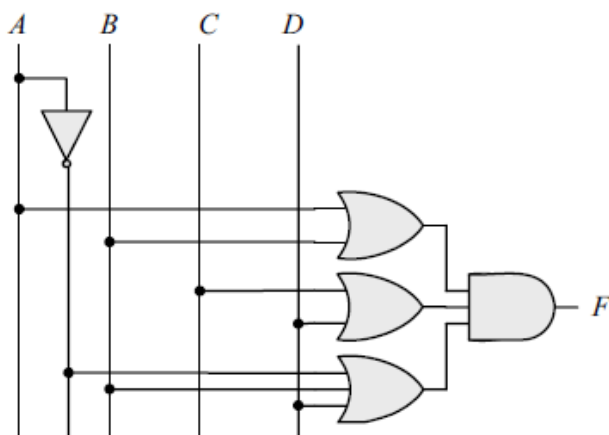

(c) $(AB + A'B')(CD' + C'D)$

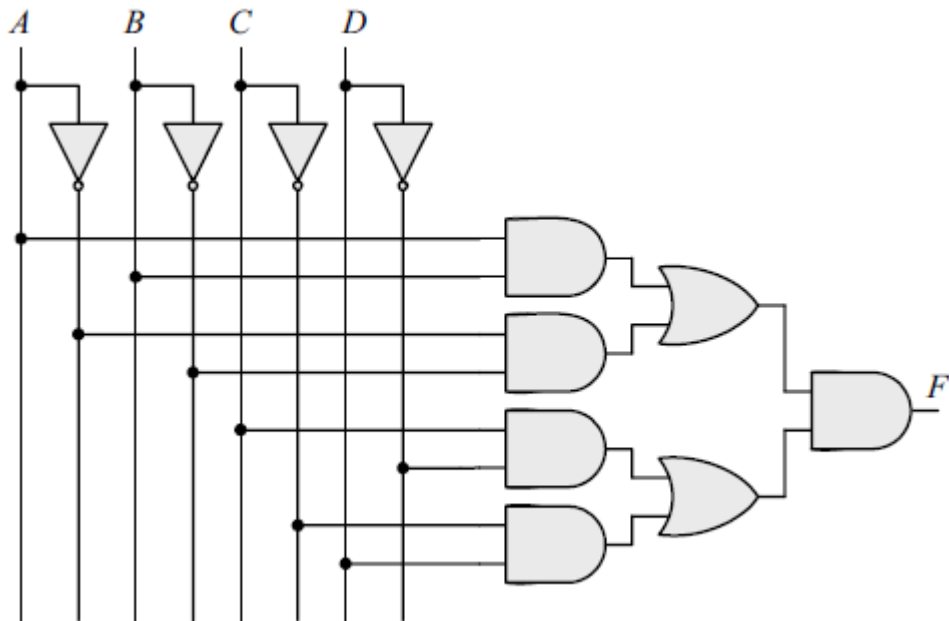

(d) $A + CD + (A + D')(C' + D)$

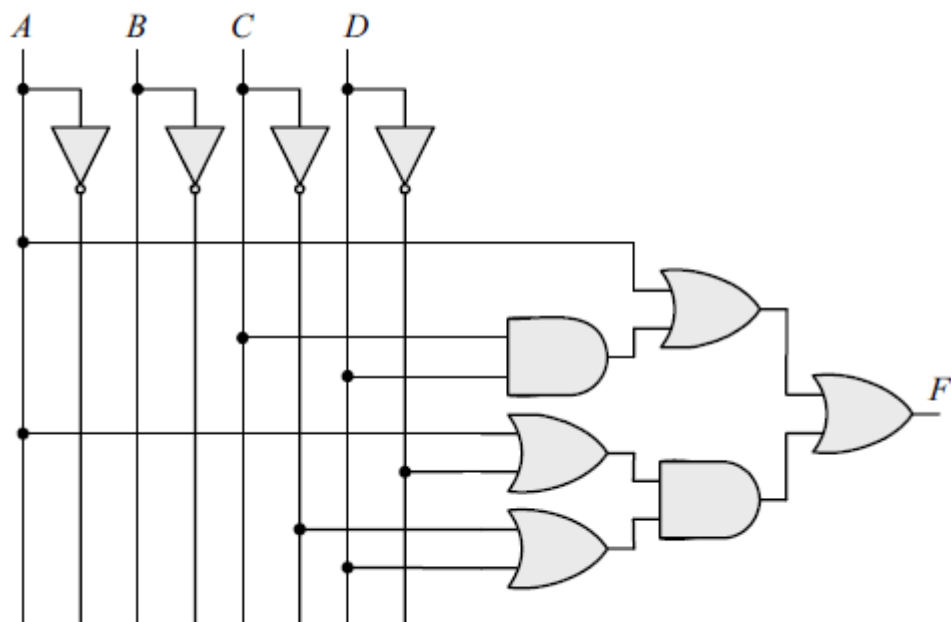

[2.26] Write the following Boolean expressions in sum of products form :

$$(b + d)(a' + b' + c)$$

$$a'b + b'b + bc + a'd + db' + dc$$

$$a'b + 0 + bc + a'd + db' + dc$$

$$a'b + bc + a'd + db' + dc$$

[2.27] Write the following Boolean expression in product of sums form:

$$a'b + a'c' + abc$$

$$= \sum(0, 2, 3, 7)$$

$$= \prod(1, 4, 5, 6)$$

$$(a+b+c')(a'+b+c)(a'+b+c')(a'+b'+c)$$