
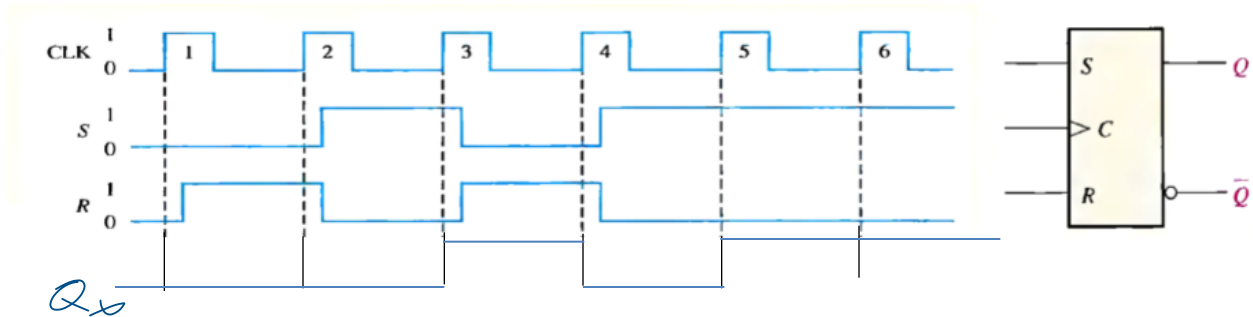


Assignment 5

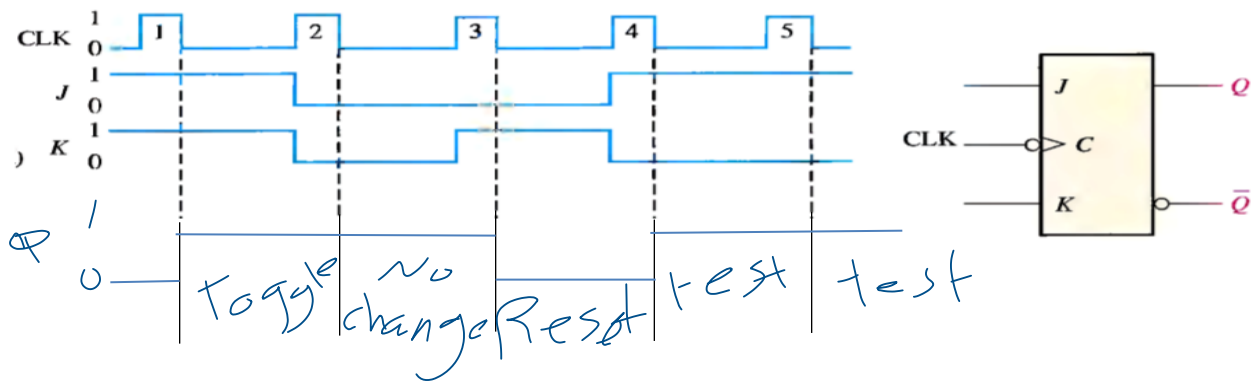
- [1] Draw the Q output waveform of the flip-flop in the following figure for the S, R, and CLK inputs. Assume that the positive edge-triggered flip-flop is initially RESET.





- [2] The waveforms in the following figure are applied to the J, K, and clock inputs as indicated. Draw the Q output waveform, assuming that the flip-flop is initially RESET.



 - [3] Draw the Q output waveform if the inputs shown in the following figure are applied to a gated D latch, which is initially RESET.



  [4] Design a 3-bit ripple up counter using positive edge trigger J-K flip-flops.



[5] Design a BCD ripple up counter using positive edge trigger J-K flip-flops.

