

Assignment 3

[1] Simplify the following Boolean functions, using three-variable maps:

(a) $F(x,y,z) = \sum(0,2,6,7)$

0 1 2 3 / 0 1
0 1 1 0

1	
1	
1	1

$=x'z' + xy$

(b) $F(x,y,z) = \sum(0,2,3,4,6)$

0 1 2 3 / 0 1
0 1 1 0

1	
1	1
1	
1	

$=z' + x'y$

(c) $F(x,y,z) = \sum(0,1,2,3,7)$

0 1 2 3 / 0 1
0 1 1 0

1	1
1	1
	1

$=x' + yz$

(d) $F(x,y,z) = \sum(3,5,6,7)$


0 1 2 3 / 0 1
0 1 1 0

	1
1	1
	1

$=xy + yz + xz$


[2] Simplify the following Boolean functions, using four-variable maps:

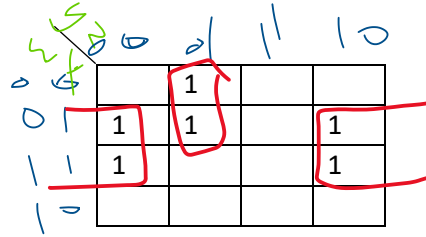(a) $F(w,x,y,z) = \sum(1,4,5,6,12,14,15)$




$=xz' + w'y'z$

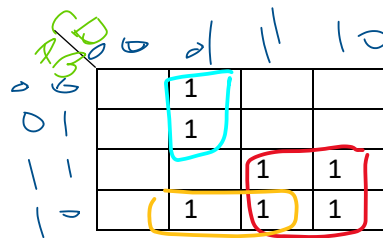(b) $F(A,B,C,D) = \sum(1,5,9,10,11,14,15)$




$=AC + AB'D + A'C'D$

(c) $F(w,x,y,z) = \sum(1,4,5,6,7,8,9)$

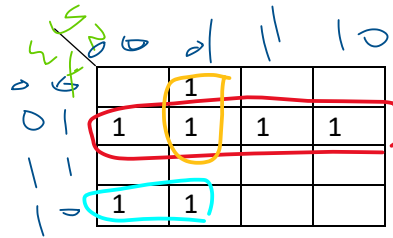

$=w'x + w'y'z + wx'y'$

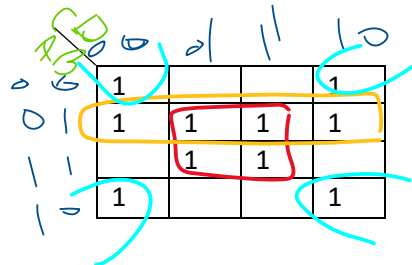(d) $F(A,B,C,D) = \sum(0,2,4,5,6,7,8,10,13,15)$



$=BD + A'B + B'D'$

[3] Simplify the following expressions to (1) sum-of-products and (2) products-of-sums:

(a) $\bar{x}\bar{z} + y\bar{z} + yz + xy$

$$= \bar{z}(\bar{x} + \bar{y} + y) + xy$$

$$= \bar{z} + xy \quad (\text{SOP})$$

$$= \bar{z} \cdot (x+y) \quad (\text{POS})$$

(b) $AC\bar{D} + \bar{C}D + A\bar{B} + ABCD$

$$= AC(\bar{D} + BD) + \bar{C}D + A\bar{B}$$

$$= AC(\bar{D} + B) + \bar{C}D + A\bar{B}$$

$$= AC\bar{D} + ACB + \bar{C}D + A\bar{B}$$

$$= A(C\bar{D} + CB + \bar{B}) + \bar{C}D$$

$$= AC + A\bar{B} + \bar{C}D \quad (\text{SOP})$$

$$= (A+C) \cdot (A + \bar{B}) \cdot (\bar{C} + D) \quad (\text{POS})$$

(c) $(A + \bar{C} + \bar{D})(\bar{A} + \bar{B} + \bar{D})(\bar{A} + B + \bar{D})(\bar{A} + B + \bar{C})$

$$= \bar{C}\bar{D} + \bar{A}\bar{C} + \bar{A}\bar{D} + B\bar{D} \quad (\text{SOP})$$

$$= (\bar{C} + \bar{D}) \cdot (\bar{A} + \bar{C}) \cdot (\bar{A} + \bar{D}) \cdot (B + \bar{D}) \quad (\text{POS})$$

(d) $AB\bar{C} + A\bar{B}D + BCD$

$$= AD + AB\bar{C} + BCD \quad (\text{SOP})$$

$$= (A+D) \cdot (A+B+\bar{C}) \cdot (B+C+D) \quad (\text{POS})$$

[4] Using K-map derive the minimum SOP expression for each of the following functions:

(a) $F = ab'c' + ab'c + abc' + abc$

	0	1
0		
1	1	1
0	1	1

$$= a$$

$$= \sum(4,5,6,7)$$


(b) $Q = c' + cd + ac + a'bc'd + abc$

$= a + c' + d$

$F = \sum(0,1,3,4,5,7,8,9,10,11,12,13,14,15)$

[5] $F(w,x,y,z) = \sum(2, 3, 6, 8, 11, 12, 14)$


(a) Show F on a K-map.

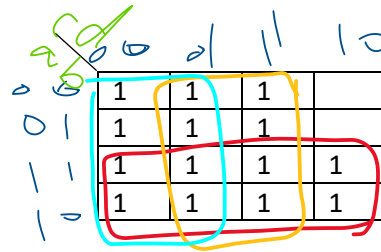

(b) Obtain a minimal sum of products expression for F.

$F = wy'z' + x'yz + xyz' + w'yz'$

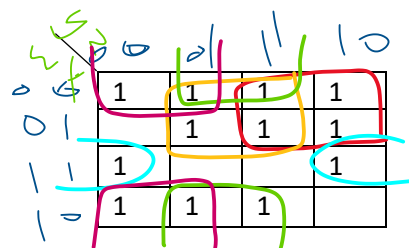(c) If the minterms: m4, m10, m13 and m15 will never occur determine a new minimal sum of products expression for F.



$= w'y + w'z + wxz' + x'y' + x'z$

[6] Convert the following Boolean function from a sum-of-products form to a simplified product-of-sums form.

$$F(w,x,y,z) = \sum(0,1,2,5,8,10,13)$$

1	1		1
	1		
			1
1			1

$$=x'z'+xy'z+w'y'z \text{ (SOP)}$$

$$=(x'+z').(x+y'+z).(w'+y'+z) \text{ (POS)}$$

[7] Simplify the following Boolean function F , together with the don't-care conditions d , and then express the simplified function in sum-of-minterms form:

$$(a) F(x,y,z) = \sum(2,3,4,6,7) \quad \text{and} \quad d(x,y,z) = \sum(0,1,5)$$

d	d
1	1
1	1
1	d

$$=1$$

$$(b) F(A,B,C,D) = \sum(0,6,8,13,14) \quad \text{and} \quad d(A,B,C,D) = \sum(2,4,10)$$

1			d
d	1	1	d
1	d	d	d
1	d	d	d

$$=CD'+B'D'+ABC'$$

(c) $F(A,B,C,D) = \sum(4,5,7,12,13,14)$ and $d(A,B,C,D) = \sum(1,9,11,15)$

$= AB + C'D + A'BC' + A'BD$

1	1	1	
1	1	d	1
	d	d	

(d) $F(A,B,C,D) = \sum(1,3,8,10,15)$ and $d(A,B,C,D) = \sum(0,2,9)$

$= B'D' + A'B' + ABCD$

d	1	1	d
		1	
1	d		1


[8] Simplify the following functions, and implement them with two-level NAND gate circuits:

(a) $F(A,B,C,D) = \overline{A}\overline{B}C + \overline{A}C + ACD + ACD + \overline{A}\overline{B}D$

$= C + \overline{A}\overline{B}D$

1		1	1
		1	1
		1	1
		1	1

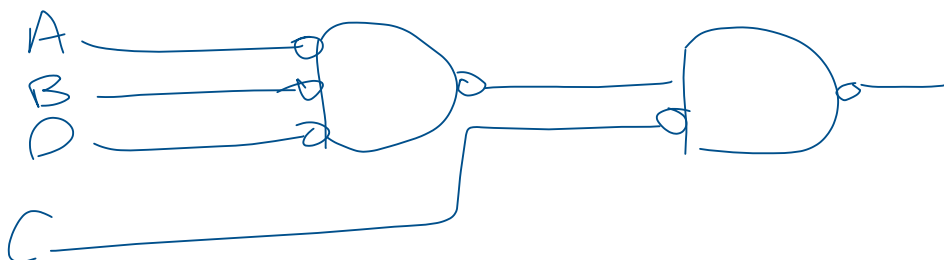$= C + \overline{A}\overline{B}D = \overline{\overline{C} \cdot (A + B + D)} = \overline{\overline{C} \cdot (A + B + D)} = \overline{\overline{C} \cdot (\overline{A} \cdot \overline{B} \cdot \overline{D})}$




(b) $F(A,B,C,D) = AB + \bar{A}BC + \bar{A}\bar{B}CD$

Handwritten Karnaugh map for $F(A,B,C,D)$ with minterms 1, 3, 5, 7 circled in red and yellow.

	0	1	1	0
0		1		
1	1	1	1	1

$= \bar{A}\bar{B}CD + AB + BC$

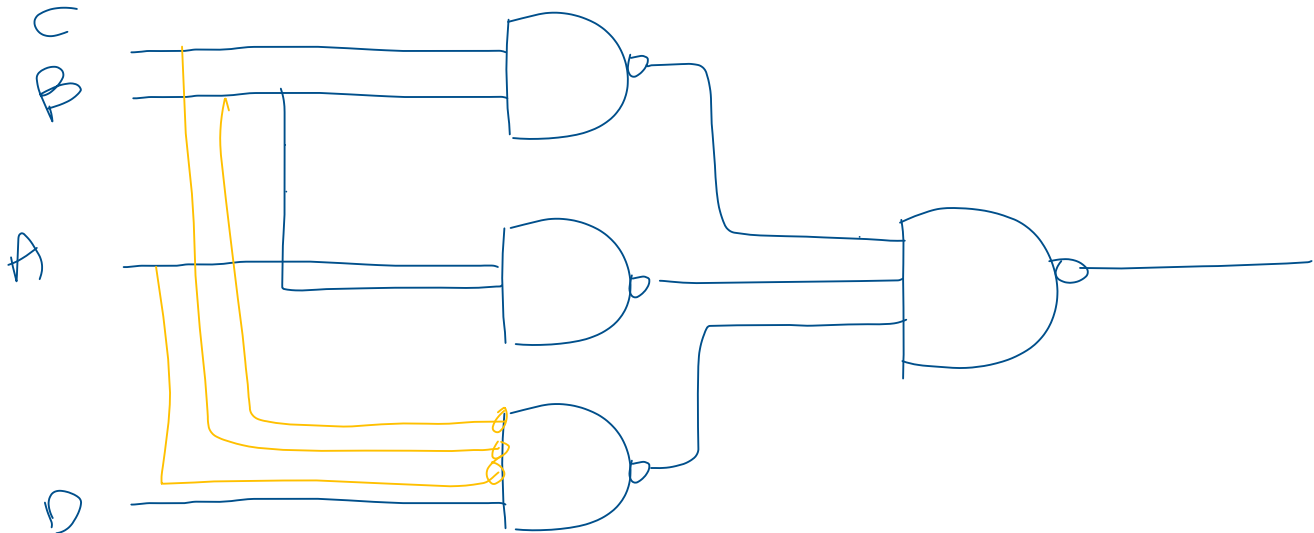$= \bar{A}\bar{B}CD + AB + BC = \overline{\overline{\bar{A}\bar{B}CD} + \overline{AB} + \overline{BC}} = (\overline{\bar{A}\bar{B}CD}) \cdot (\overline{AB}) \cdot (\overline{BC})$




[9] Simplify the following functions, and implement them with two-level NOR gate circuits:

(a) $F = w\bar{x} + \bar{y}\bar{z} + \bar{w}y\bar{z}$

Handwritten Karnaugh map for $F(w,x,y,z)$ with minterms 2, 3, 6, 7 circled in red and yellow.

	0	1	1	0
1	0	0	1	
1	0	0	1	
1	0	0	0	
1	1	1	1	
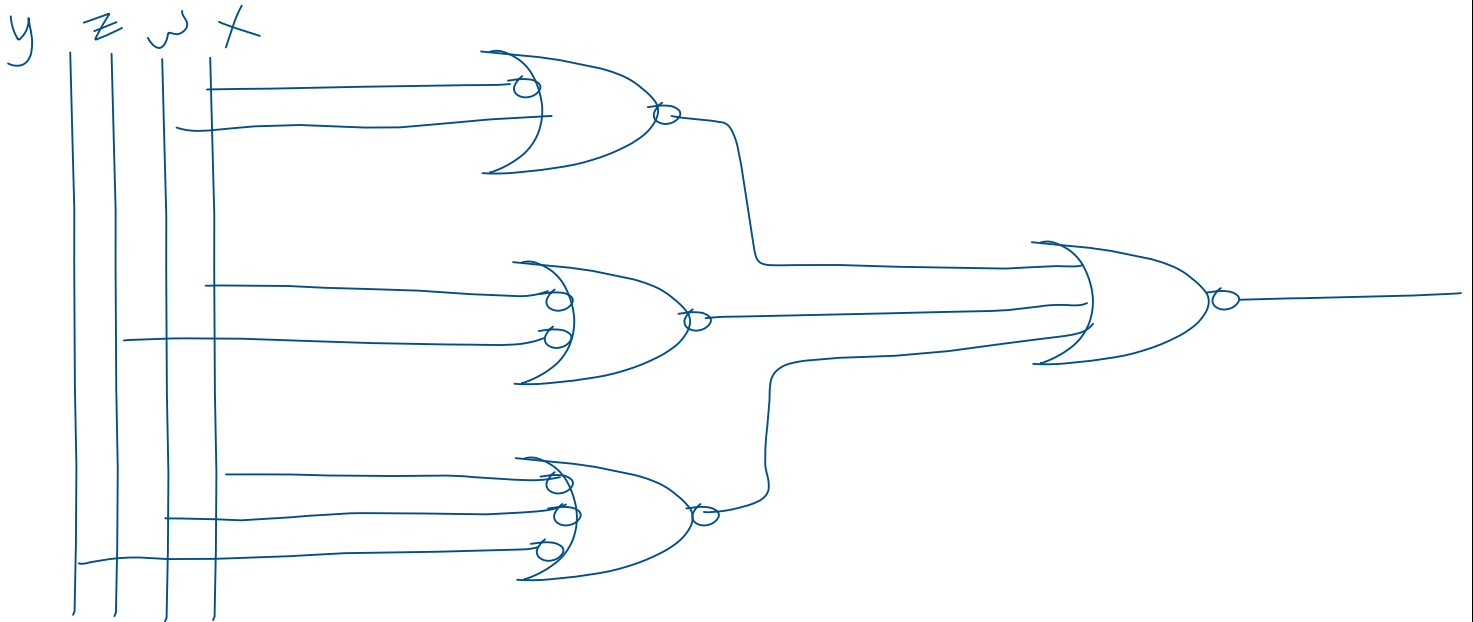
$$= \overline{\overline{(\bar{z} + w)(\bar{x} + \bar{z})(\bar{w} + \bar{x} + \bar{y})}} = \overline{(\bar{z} + w) + (\bar{x} + \bar{z}) + (\bar{w} + \bar{x} + \bar{y})}$$




(b) $F(w,x,y,z) = \Sigma(1,2,13,14)$

	0	1	0	1
0	0	0	0	0
1	0	1	0	1
0	0	0	0	0


$$= (y + x)(\bar{y} + \bar{z}) + (w + \bar{x})(\bar{w} + x) = \overline{\overline{(y + x)(\bar{y} + \bar{z}) + (w + \bar{x})(\bar{w} + x)}}$$
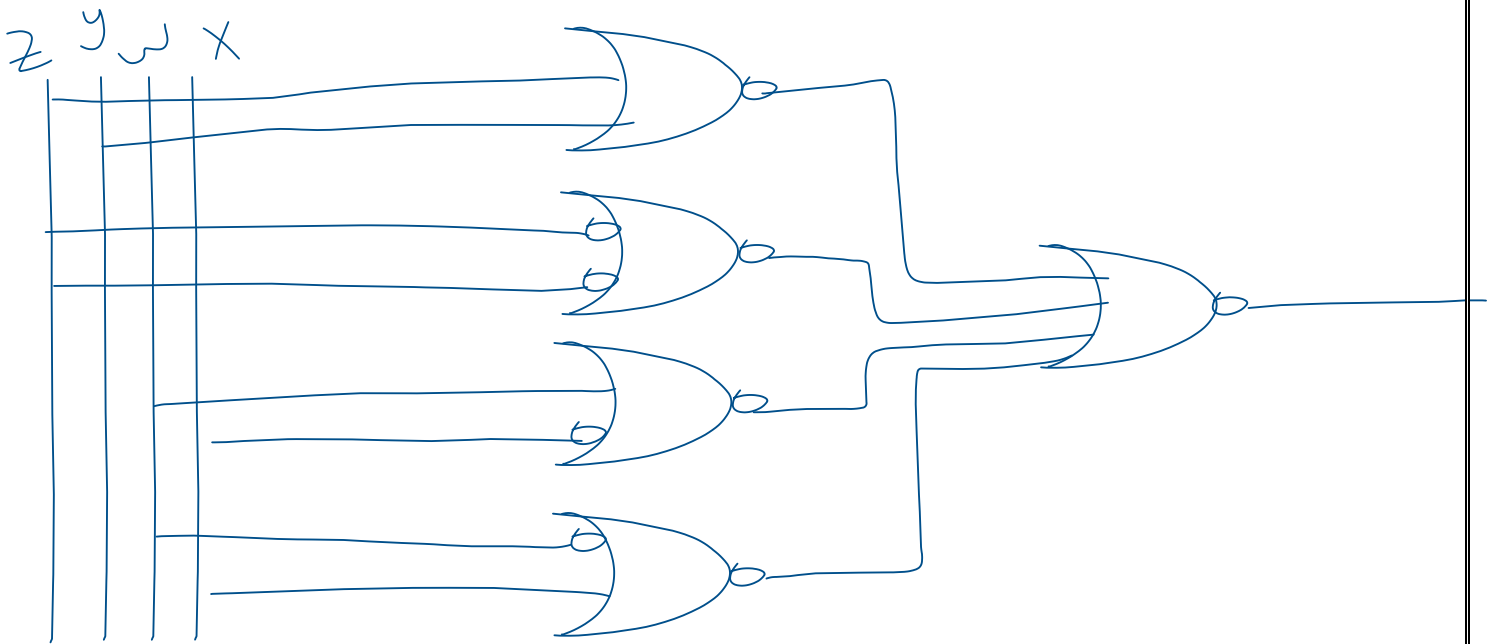
$$= \overline{\overline{(y + x)(\bar{y} + \bar{z})} + \overline{\overline{(w + \bar{x})(\bar{w} + x)}}}$$



[10] (a) Implement the following function using NAND gates with a fan in of 2.
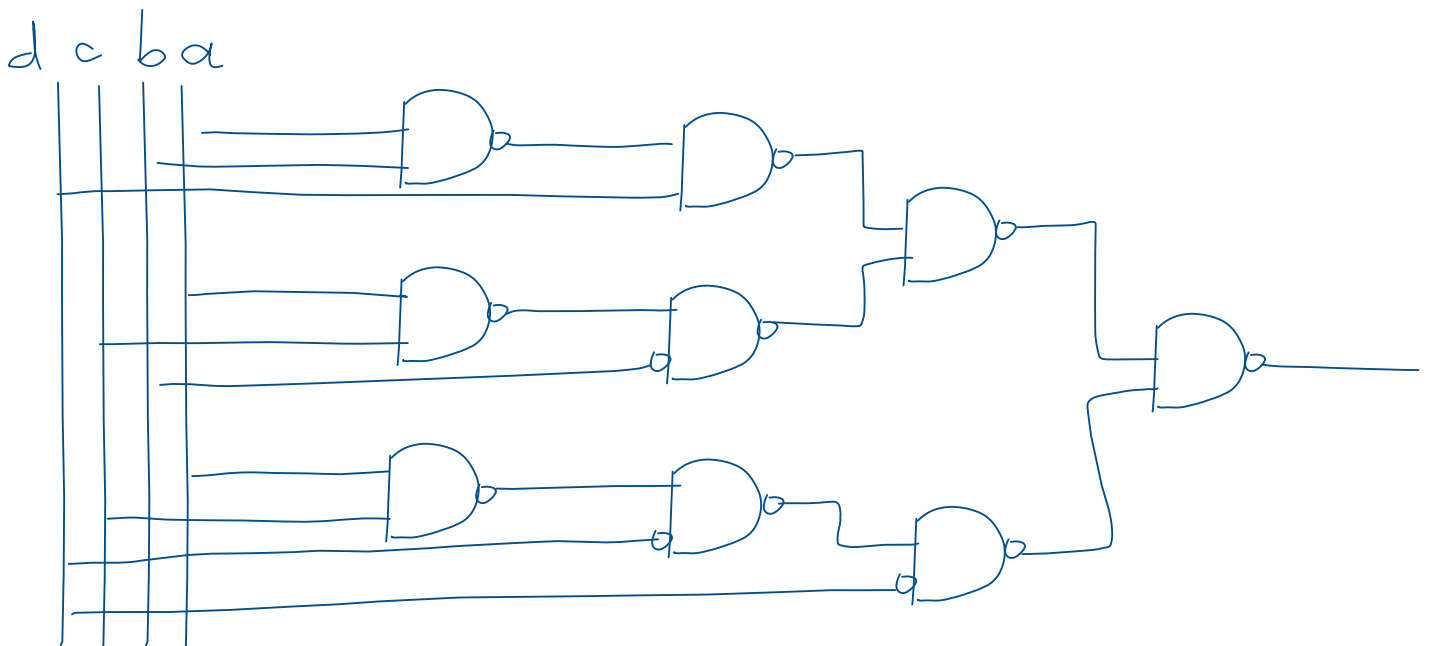
$$\begin{aligned}
 F &= (ab + d')(ac + b) + (ac + b)d \\
 &= \overline{(ab + d')(ac + b)} + (ac + b)d \\
 &= \overline{(ab + d')(ac + b)} + \overline{(ac + b)}d \\
 &= \overline{(\overline{ab} + d)(\overline{ac} + \overline{b})} + (\overline{ac} + \overline{b})d
 \end{aligned}$$



(b) Simplify the above function and implement using NAND gates with a fan in of 2.


$$= abc + ab + ac\bar{d} + \bar{d}b + acd + db$$

$$= ab(c + 1) + ac(\bar{d} + d) + b(\bar{d} + d)$$


$$= ab + ac + b$$

$$= b(a+1) + ac$$
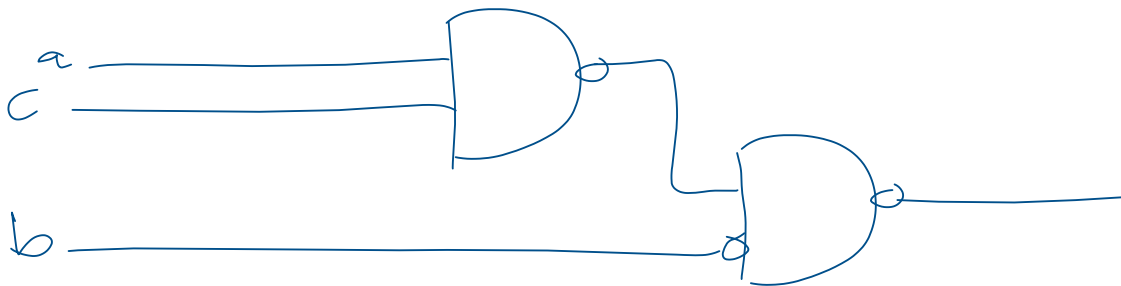
$$= b + ac = \overline{\overline{b} + \overline{ac}} = \overline{\overline{b} \cdot \overline{ac}}$$



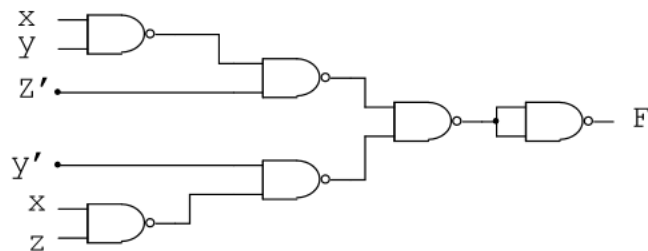[11] Determine the value of F in a standard form:



$$= ((xy) \cdot \bar{z}) \cdot ((xz) \cdot \bar{y}) = (\overline{(xy) \cdot \bar{z}}) \cdot (\overline{(xz) \cdot \bar{y}}) = xyz + \bar{y}\bar{z}$$