



Assignment 2

[1] Consider a Boolean Algebra $\langle B, +, \cdot, 0, 1 \rangle$ Show that

(a) $x \cdot y + x' \cdot z + yz = x \cdot y + x' \cdot z$

$$xy + x'z + yz = xy + x'z + (1)yz$$

$$= xy + x'z + (x + x')yz$$

$$= xy + x'z + (xyz + x'yz)$$

$$= (xy + xyz) + (x'z + x'yz)$$

$$= xy(1 + z) + x'z(1 + y)$$

$$= xy(1) + x'z(1)$$

$$= xy + x'z$$

(b) $(a + b)'(a' + b)' = 0$

$$(a + b)'(a' + b)'$$

$$= (a' \cdot b') (a \cdot b)$$

$$= a' \cdot a \cdot b'$$

$$= 0 \cdot b'$$

$$= 0$$

[2] Algebraically simplify the following expressions:

(a) $F = abc + a'bc + a'b'c + abc' + a'b'c'$

$$= bc(a' + a) + a'c(b' + b) + abc'$$

$$= bc + a'c + abc'$$

(b) $F = y(wz' + wz) + xy$

$$= yw(z' + z) + xy$$

$$= yw + xy$$

$$= y(w + x)$$

[3] Simplify the following Boolean expressions to a minimum number of literals :

(a) $xy + x\bar{y}$

$$= x(y + \bar{y})$$

$$= x(1) = x$$

$$\begin{aligned}
 \text{(b)} \quad & (x + y)(x + \bar{y}) \\
 &= x + xy + x\bar{y} + y\bar{y} \\
 &= x(1 + y + \bar{y}) + 0 \\
 &= x
 \end{aligned}$$

$$\begin{aligned}
 \text{(c)} \quad & xyz + \bar{x}y + xy\bar{z} \\
 &= xy(z + \bar{z}) + \bar{x}y \\
 &= xy(1) + \bar{x}y \\
 &= y(x + \bar{x}) \\
 &= y
 \end{aligned}$$

$$\begin{aligned}
 \text{(d)} \quad & (\overline{A + B})(\bar{A} + \bar{B}) \\
 &= \overline{AB}(\bar{A} + \bar{B}) \\
 &= \overline{AAB} + \overline{AB\bar{B}} \\
 &= \overline{AB} + \overline{AB} \\
 &= \overline{AB}
 \end{aligned}$$

[4] Reduce the following Boolean expressions to the indicated number of literals :

$$\begin{aligned}
 \text{(a)} \quad & \bar{A}\bar{C} + ABC + A\bar{C} \quad \text{to three literals.} \\
 &= \bar{C}(\bar{A} + A) + ABC \\
 &= \bar{C} + ABC \\
 &= \bar{C} + AB
 \end{aligned}$$

$$\begin{aligned}
 \text{(b)} \quad & \overline{(\bar{x}\bar{y} + z)} + z + xy + wx \quad \text{to three literals.} \\
 &= (\bar{x}\bar{y})\bar{z} + z + xy + wz \\
 &= [(x + y)\bar{z} + z] + xy + wz \\
 &= (z + \bar{z})(z + x + y) + xy + wz \\
 &= z + wz + x + xy + y \\
 &= z(1 + w) + x(1 + y) + y \\
 &= x + y + z
 \end{aligned}$$

$$\begin{aligned}
 \text{(c)} \quad & \bar{A}B(\bar{D} + \bar{C}D) + B(A + \bar{A}CD) \quad \text{to one literals.} \\
 &= B(AD + \bar{A}\bar{C}D + A + \bar{A}CD) \\
 &= B(\bar{A}\bar{D} + A + \bar{A}D(C + \bar{C})) \\
 &= B(A + \bar{A}(\bar{D} + D)) \\
 &= B(A + \bar{A}) \\
 &= B
 \end{aligned}$$

$$(d) (\bar{A} + C)(\bar{A} + \bar{C})(A + B + \bar{C}D)$$

to four literals.

$$=(\bar{A}\bar{A} + \bar{A}\bar{C} + \bar{A}C + C\bar{C})(A + B + \bar{C}D)$$

$$=(\bar{A} + \bar{A}\bar{C} + \bar{A}C)(A + B + \bar{C}D)$$

$$= \bar{A}(\bar{A} + \bar{C} + C)(A + B + \bar{C}D)$$

$$=\bar{A}(\bar{A}+1)(A + B + \bar{C}D)$$

$$=(\bar{A}\bar{A} + \bar{A}B + \bar{A}\bar{C}D)$$

$$= \bar{A}B + \bar{A}\bar{C}D$$

$$= \bar{A}(B + \bar{C}D)$$

[5] Find the complement of the following expressions :

$$(a) x\bar{y} + \bar{x}y$$

$$F=(x\bar{y} + \bar{x}y)'$$

$$=(x'+y).(x+y')$$

$$=x.x' + x'.y' + y.x + y.y'$$

$$= 0 + x'y' + x.y + 0$$

$$=x'y' + xy$$

$$(b) (a + c)(a + \bar{b})(\bar{a} + b + \bar{c})$$

$$= \overline{[(a + c)(a + \bar{b})(\bar{a} + b + \bar{c})]}$$

$$= \overline{(a + c)} + \overline{(a + \bar{b})} + \overline{(\bar{a} + b + \bar{c})}$$

$$= (\bar{a} . \bar{c}) + (\bar{a} . b) + (a . \bar{b} . c)$$

$$(c) z + \bar{z}(\bar{v}w + xy)$$

$$= \overline{z + \bar{z}(\bar{v}w + xy)}$$

$$= \bar{z} . [z + (\bar{v}w + xy)]$$

$$= \bar{z} . [z + ((v + \bar{w}).(\bar{x} + \bar{y}))]$$

$$= z\bar{z} + \bar{z} . (v + \bar{w}).(\bar{x} + \bar{y})$$

$$= 0 + \bar{z} . (v + \bar{w}).(\bar{x} + \bar{y})$$

$$= \bar{z} . (v + \bar{w}).(\bar{x} + \bar{y})$$

$$(d) (w + \bar{y}z)(x + \bar{w}z)$$

$$= \overline{(w + \bar{y}z)(x + \bar{w}z)}$$


$$= \overline{(w + \bar{y}z)} + \overline{(x + \bar{w}z)}$$

$$= (\bar{w} . ((\bar{y})z)) + (\bar{x} . (\bar{w}z))$$

$$= (\bar{w} . (y + \bar{z})) + (\bar{x} . (w + \bar{z}))$$

$$= \bar{w}\bar{y} + \bar{w}\bar{z} + \bar{x}w + \bar{x}\bar{z}$$

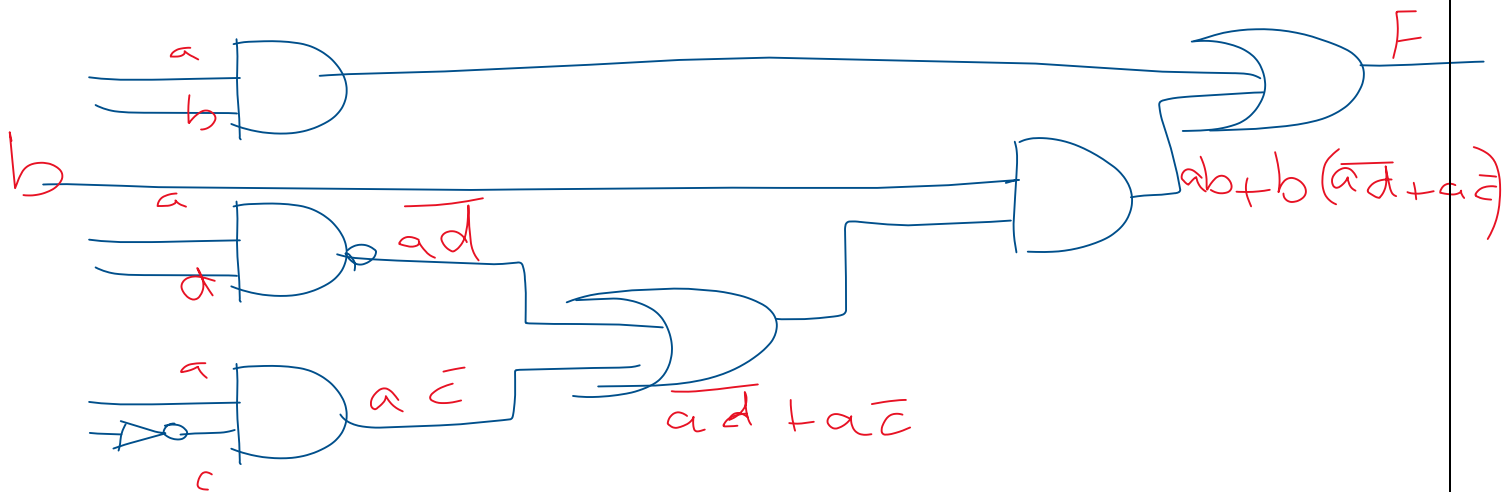
[6] Given $F = ab + b(\overline{a}d + a\overline{c})$ implement it with AND, OR and inverter gates.



[7] Implement the Boolean function


$$F = xy + \overline{y}z$$

(a) With AND, OR, and inverter gates

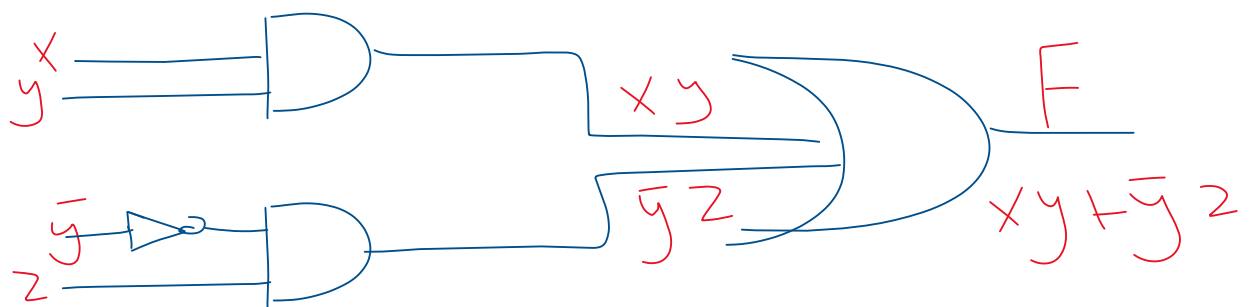

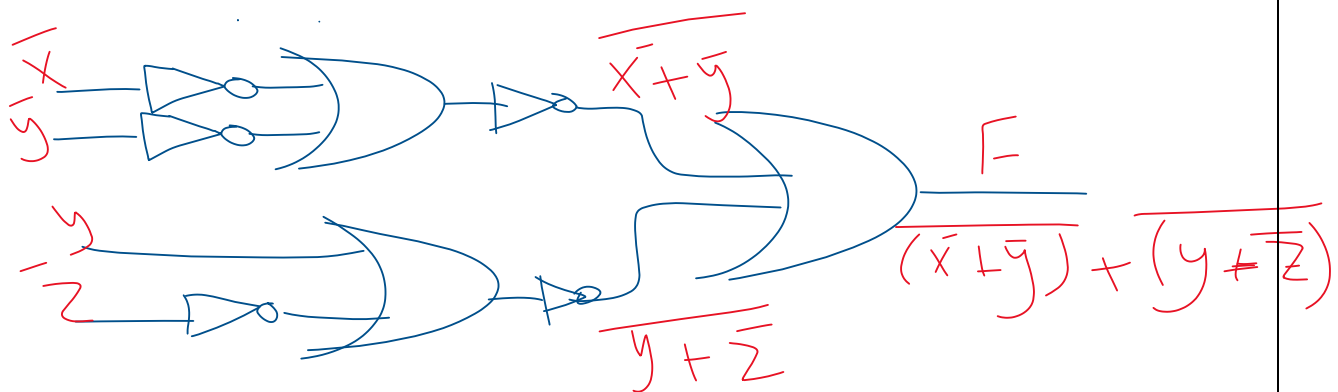
(b) With OR and inverter gates

$$= \overline{(\overline{x} + \overline{y})} + \overline{(y + \overline{z})}$$



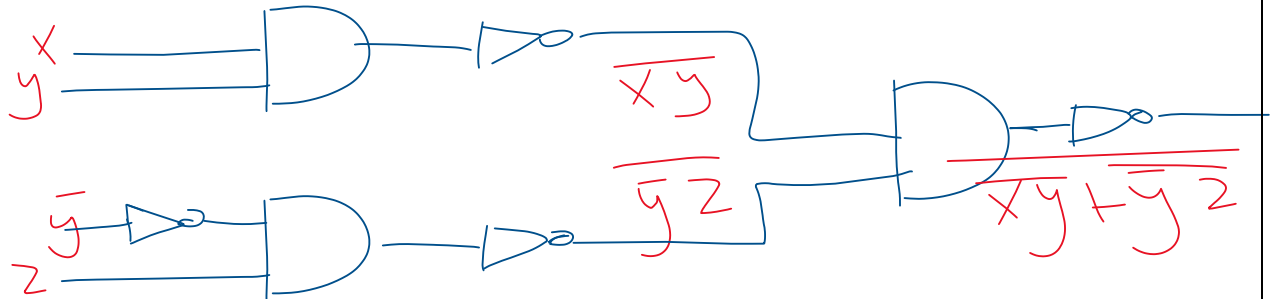
(c) With AND and inverter gates

$$= \overline{(xy) \cdot (\overline{y}z)}$$



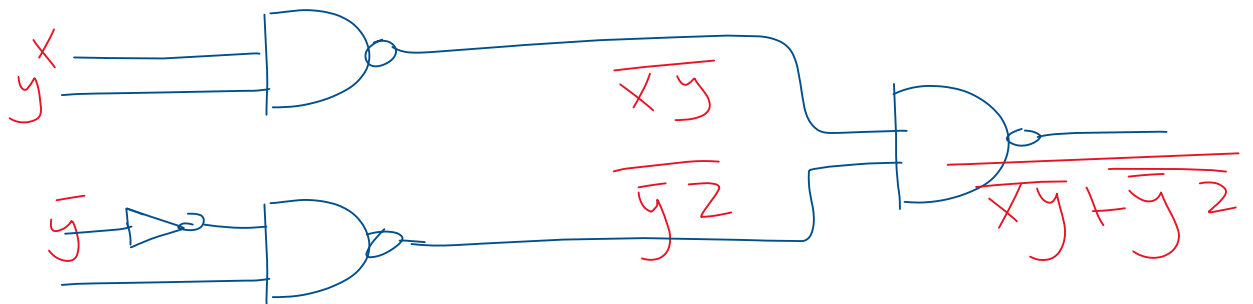
(d) With NAND and inverter gates

$$= \overline{(xy) \cdot (\overline{y}z)}$$



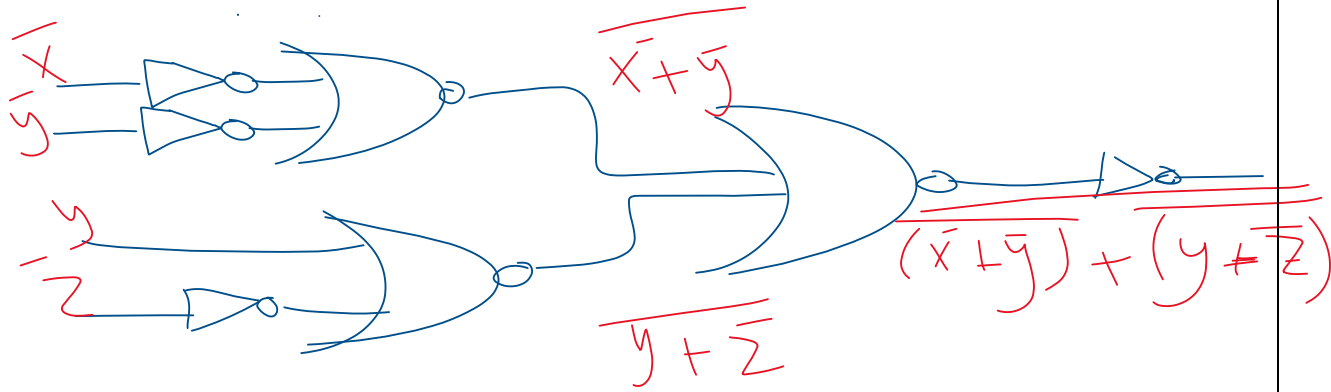(e) With NOR and inverter gates

$$= \overline{(\bar{x} + \bar{y})} + \overline{(y + \bar{z})} = \overline{(\bar{x} + \bar{y})} + \overline{(y + \bar{z})}$$



[8] Express the following function as a sum of minterms and as a product of $F(A,B,C,D) = \bar{B} D + \bar{A} D + BD$

$$= D(\bar{B} + \bar{A} + B) = D\bar{A}$$

A	\bar{A}	B	C	D	$F=D\bar{A}$
0	1	0	0	0	0
0	1	0	0	1	1
0	1	0	1	0	0
0	1	0	1	1	1
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	0
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	0

$$F(A, B, C, D) = \Sigma(1,3,5,7)$$

$$F(A, B, C, D) = \Pi(0,2,4,6,8,9,10,11,12,13,14,15)$$

[9] Express the complement of the following functions in sum-of-minterms form :

(a) $F(A,B,C,D) = \Sigma(2,4,7,10,12,14)$

$$\bar{F}(A,B,C,D) = \Sigma(0,1,3,4,5,6,8,9,11,13,15)$$

(b) $F(x,y,z) = \Pi(3,5,7)$

$$\bar{F}(x,y,z) = \Sigma(3,5,7)$$

[10] Convert each of the following to the other canonical form :

(a) $F(x,y,z) = \sum(1,3,5)$

$F(x,y,z) = \prod(0,2,4,6,7)$

(b) $F(A,B,C,D) = \prod(3, 5, 8, 11)$

$F(A,B,C,D) = \sum(0,1,2,4,6,7,9,10,12,13,14,15)$

[11] Convert each of the following expressions into sum of products and product of sums :

(a) $F = (AB + C)(B + \bar{C}D)$

$= ABB + AB\bar{C}D + CB + C\bar{C}D$

$= AB + AB\bar{C}D + CB + 0$

$= AB(1 + \bar{C}D) + CB$

$= AB + CB \quad (\text{SOP})$

$= B(A+C) \quad (\text{POS})$

(b) $F = \bar{x} + x(x + \bar{y})(y + \bar{z})$

$= \bar{x} + \bar{z}x + xy + zx\bar{y} + xy\bar{y}$

$= \bar{x} + \bar{z}x(1 + \bar{y}) + xy$

$= \bar{x} + \bar{z}x + xy$

$= \bar{x} + \bar{z}x + \bar{x} + xy$

$= \bar{x} + \bar{z} + \bar{x} + y$

$= \bar{x} + \bar{y} + z \quad (\text{SOP}) \& (\text{POS})$

Where we used

$\bar{x} + xy$

$= \bar{x}(y + \bar{y}) + xy$

$= x(y + y + \bar{y}) + xy$

$= \bar{x}(y + \bar{y}) + \bar{x}y + xy$

$= \bar{x} + (\bar{x} + x)y$

$= \bar{x} + y$

[12] Express the following functions as CSOP and CPOS expressions:

(a) $F(x,y,z) = (x + y' + z)(x + z') + yz$ in terms of x, y, and z

$= xx + x\bar{z} + \bar{y}x + \bar{y}\bar{z} + zx + z\bar{z} + yz$

$= x(1 + \bar{z} + \bar{y}) + \bar{y}z + zx + yz$

$= x + \bar{y}z + zx + yz$

$= x + z(\bar{y} + y + x)$

$= x + z$

(b) $F(w, x, y, z) = \overline{xy} (wz + \overline{w} \overline{z}) (w + \overline{xz})$


in terms of w, x, y, and z

$= \overline{xy} (1) (w + \overline{xz})$

$= \overline{xy} (w + \overline{xz})$

$= \overline{xy} w + \overline{xyz}$

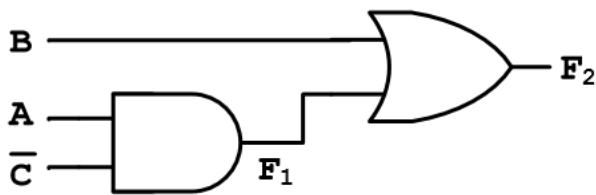[13] Given the following pulse trains for A, B and C, draw the pulse trains for F1 and F2.



Draw the answers here

